

Laboratory Exercise 7 - Week 2

Applications of Counters

This week focuses on applications of counters, including timing generation and controlling display sequences.

Part IV

Design and implement a circuit that successively flashes digits 0 through 9 on the 7-segment display HEX0. Each digit should be displayed for about one second. Use a counter to determine the one-second intervals. The counter should be incremented by the 50-MHz clock signal provided on the DE0-CV board. For the output, you can use the 7-segment decoder from previous exercises.

 


Figure 4: Making a slow counter to drive a display.

 


Figure 5: Timing diagram for the pulse signal (50 MHz clock).

Do not derive any other clock signals in your design—make sure that all flip-flops in your circuit are clocked directly by the 50-MHz clock signal. A partial design of the required circuit is shown in Figure 4, and its corresponding timing diagram is shown in Figure 5. The figure shows how a large bit-width counter can be used to produce an enable signal for a smaller counter.

For reference, an example of a counter specified using a generic parameter n is shown in Figure 6.

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3  USE ieee.numeric_std.all;
4
5  ENTITY counter IS
6      GENERIC ( n : INTEGER := 4 );
7      PORT ( Clock, Clear, Enable : IN STD_LOGIC;
8            Q : OUT UNSIGNED(n-1 DOWNT0 0));
9  END counter;
10
11  ARCHITECTURE Behavior OF counter IS
12      SIGNAL value : UNSIGNED(n-1 DOWNT0 0);
13  BEGIN
14      PROCESS ( Clock, Clear )
15      BEGIN
16          IF Clear = '0' THEN
17              value <= (OTHERS => '0');
18          ELSIF RISING_EDGE(Clock) THEN
19              IF Enable = '1' THEN
20                  value <= value + 1;
21              END IF;
22          END IF;
23      END PROCESS;
24      Q <= value;
25  END Behavior;

```

Figure 6: A generic n-bit counter.

Part V

Design and implement a circuit that displays a word on three 7-segment displays HEX2-0. The word to be displayed for your DE0-CV board is "dE0". Make the letters rotate from right to left in intervals of about one second.

Clock Cycle	HEX2	HEX1	HEX0
0	d	E	0
1	E	0	d
2	0	d	E

Table 1: Rotating pattern.

The specific rotation pattern you need to implement is detailed in Table 1.

 


Figure 7: Block diagram for rotating word.

A block diagram corresponding to this circuit is shown in Figure 7.

There are many ways to design the required circuit. One solution is to re-use the VHDL code designed in Laboratory Exercise 1, Part V. Using that code, the main change needed is to replace the two switches that were used to select the characters being rotated on the displays with a 2-bit counter that increments at one-second intervals. Note that the counter for this circuit must also use the 50-MHz clock signal.

For reference, an example of a 2-bit wide 4-to-1 multiplexer is shown in Figure 8.

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3
4  ENTITY mux_2bit_4to1 IS
5      PORT ( S : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
6            U, V, W, X : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
7            M : OUT STD_LOGIC_VECTOR(1 DOWNTO 0));
8  END mux_2bit_4to1;
9
10 ARCHITECTURE Behavior OF mux_2bit_4to1 IS
11 BEGIN
12     PROCESS ( S, U, V, W, X )
13     BEGIN
14         CASE S IS
15             WHEN "00" => M <= U;
16             WHEN "01" => M <= V;
17             WHEN "10" => M <= W;
18             WHEN "11" => M <= X;
19             WHEN OTHERS => M <= (OTHERS => '0');
20         END CASE;
21     END PROCESS;
22 END Behavior;

```

Figure 8: A 2-bit wide 4-to-1 multiplexer.

For reference, an example of a decoder that outputs "d", "E", "0", and blank space is shown in Figure 9.

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3
4  ENTITY hex7seg IS
5      PORT ( hex : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
6            display : OUT STD_LOGIC_VECTOR(0 TO 6));
7  END hex7seg;
8
9  ARCHITECTURE Behavior OF hex7seg IS
10 BEGIN
11     PROCESS ( hex )
12     BEGIN
13         CASE hex IS
14             WHEN "00" => display <= "1000010"; -- d
15             WHEN "01" => display <= "0110000"; -- E
16             WHEN "10" => display <= "0000001"; -- 0
17             WHEN OTHERS => display <= "1111111"; -- Blank
18         END CASE;
19     END PROCESS;
20 END Behavior;

```

Figure 9: A decoder for d, E, 0, and blank.

Part VI

Augment your circuit from Part V so that it can rotate the word "dE0" over all 6 7-segment displays on your DE0-CV board (HEX5-0). The shifting pattern is shown in Table 2. Similar to Part V, the counter for this circuit must also use the 50-MHz clock signal.

Clock Cycle	HEX5	HEX4	HEX3	HEX2	HEX1	HEX0
0				d	E	0
1			d	E	0	
2		d	E	0		
3	d	E	0			
4	E	0				d
5	0				d	E

Table 2: Rotating the word dE0 on six displays.

 


Figure 10: Rotating the word over all displays.

The block diagram for rotating the word across all displays is shown in Figure 10. Implement the circuit and demonstrate its operation on the DE0-CV board.

Updated By: R. Sutthaweeikul
Release Date: 2026-01-02